

day 3

1) $F(A, B, C) = \bar{A}C + B\bar{C}$
convert into canonical

$F = \bar{A}C + B\bar{C}$



$F = \bar{A}C(B + \bar{B}) + B\bar{C}(A + \bar{A})$

$F = \bar{A}CB + \bar{A}C\bar{B} + B\bar{C}A + B\bar{C}\bar{A}$

Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

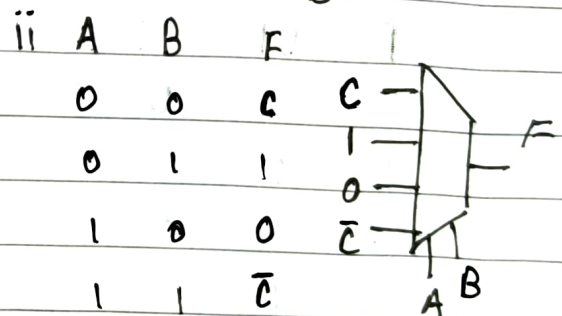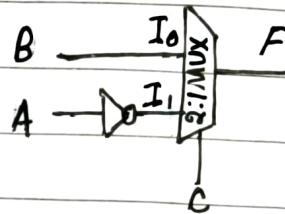i) looking at the equation: $\bar{A}C + B\bar{C}$
 $\downarrow$ $C=0 \therefore F=B$
 $\downarrow$ $C=1 \therefore F=\bar{A}$




b) $F(P, Q, R) = \bar{P}\bar{R} + Q\bar{R} + \bar{P}Q$

$F = \bar{P}\bar{R}Q + \bar{P}\bar{R}\bar{Q} + \underline{PQ\bar{R}} + \underline{PQ\bar{R}} + \bar{P}RQ + \bar{P}\bar{R}Q$

$F = \bar{R}(\bar{P}Q + \bar{P}\bar{Q} + P\bar{Q}) + R(\bar{P}Q)$


$\bar{R}(\bar{P} + Q) + R(\bar{P}Q) \therefore$ Taking $\bar{R}$ as the select line

i)

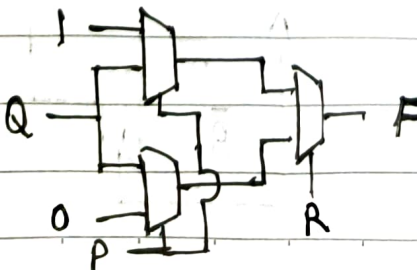

ii)

P	Q	F
0	0	$\bar{R}$
0	1	1
1	0	0
1	1	R

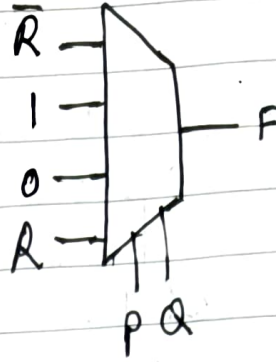

2.) Full adder - using 2:1 MUX


S, Car $\Rightarrow$ output
A, B, Cin $\Rightarrow$ Input

$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = AB + C_{in}(A \oplus B)$$

A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum:

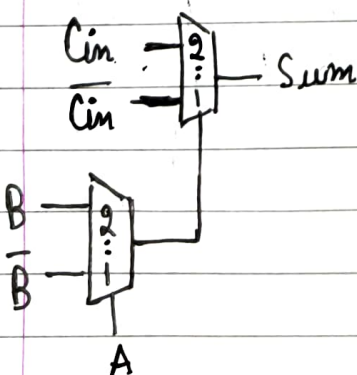

Carry:

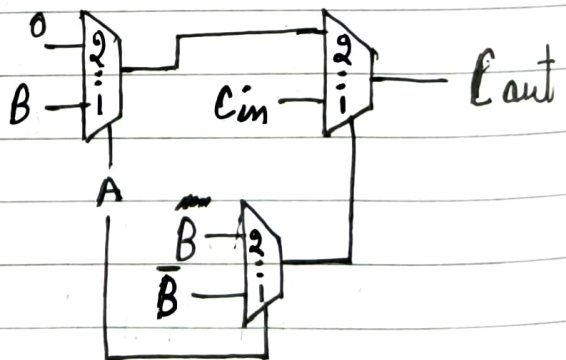

$$3.) f(a,b,c,d) = \sum(2,4,5,6,10) + D(12,13,14,15)$$

ab \ cd		cd			
		00	01	11	10
G ₂	00	0	1	3	2
	01	1	4	5	6
	11	X	X	X	X
	10	8	9	11	10

using K-MAP

$$f = b\bar{c} + \bar{c}d ; \text{ Let } a, b \text{ be the select lines}$$

